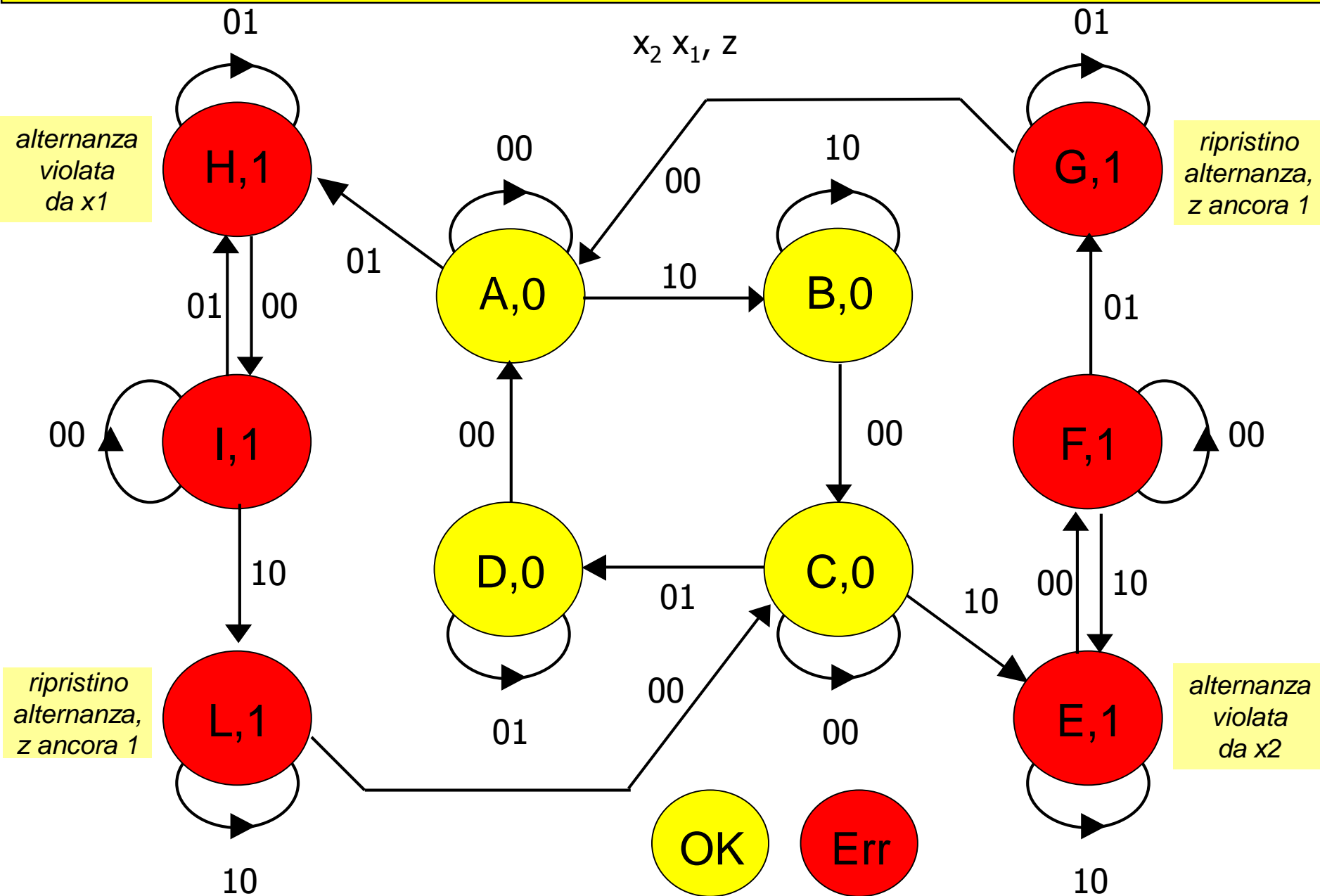


# Esercizio 1.1



# Esercizio 1.2 – TdF automa primitivo

		$x_2 \ x_1$			
		00	01	11	10
s.p.	A	A,0	H,-	-, -	B,0
	B	C,0	-, -	-, -	B,0
	C	C,0	D,0	-, -	E,-
	D	A,0	D,0	-, -	-, -
	E	F,1	-, -	-, -	E,1
	F	F,1	G,1	-, -	E,1
	G	A,-	G,1	-, -	-, -
	H	I,1	H,1	-, -	-, -
	I	I,1	H,1	-, -	L,1
	L	C,-	-, -	-, -	L,1

s.f., z

# Esercizio 1.2 – TdF minima


CMC = {A}, {B}, {C},  
{D}, {EF}, {G}, {HI}, {L}

s.p.

	$x_2 \ x_1$			
	00	01	11	10
A	A,0	h,-	-, -	B,0
B	C,0	-, -	-, -	B,0
C	C,0	D,0	-, -	e,-
D	A,0	D,0	-, -	-, -
e=EF	e,1	G,1	-, -	e,1
G	A,-	G,1	-, -	-, -
h=HI	h,1	h,1	-, -	L,1
L	C,-	-, -	-, -	L,1

s.f., z

# Esercizio 1.3

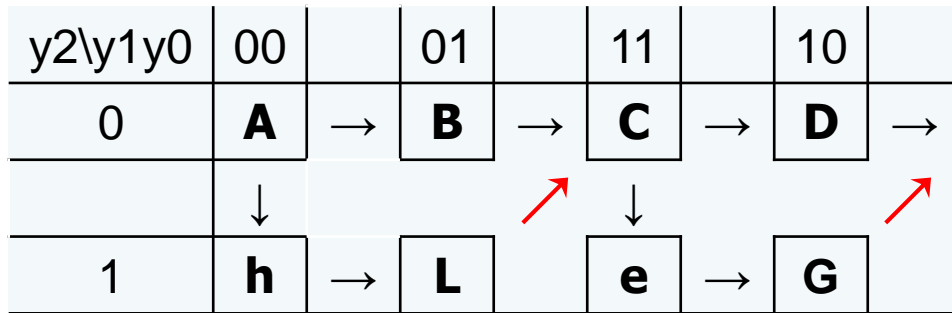

**Possibili corse critiche:**  
**L → C, risolvibile passando per B**  
**G → A, risolvibile passando per D**

s.p.

	x <sub>2</sub> x <sub>1</sub>			
	00	01	11	10
A	A,0	h,-	-, -	B,0
B	C,0	-, -	-, -	B,0
C	C,0	D,0	-, -	e,-
D	A,0	D,0	-, -	-, -
e=EF	e,1	G,1	-, -	e,1
G	D,-	G,1	-, -	-, -
h=HI	h,1	h,1	-, -	L,1
L	B,-	-, -	-, -	L,1


s.f., z

# Esercizio 1.3 - TdT

		$x_2 x_1$			
		00	01	11	10
$y_2 y_1 y_0$	A=000	000,0	100,-	-, -	001,0
	B=001	011,0	-, -	-, -	001,0
	C=011	011,0	010,0	-, -	111,-
	D=010	000,0	010,0	-, -	-, -
	h=100	100,1	100,1	-, -	101,1
	L=101	001,-	-, -	-, -	101,1
	e=111	111,1	110,1	-, -	111,1
	G=110	010,-	110,1	-, -	-, -

$y_2 y_1 y_0, z$


# Esercizio 1.4 – Sintesi combinatoria

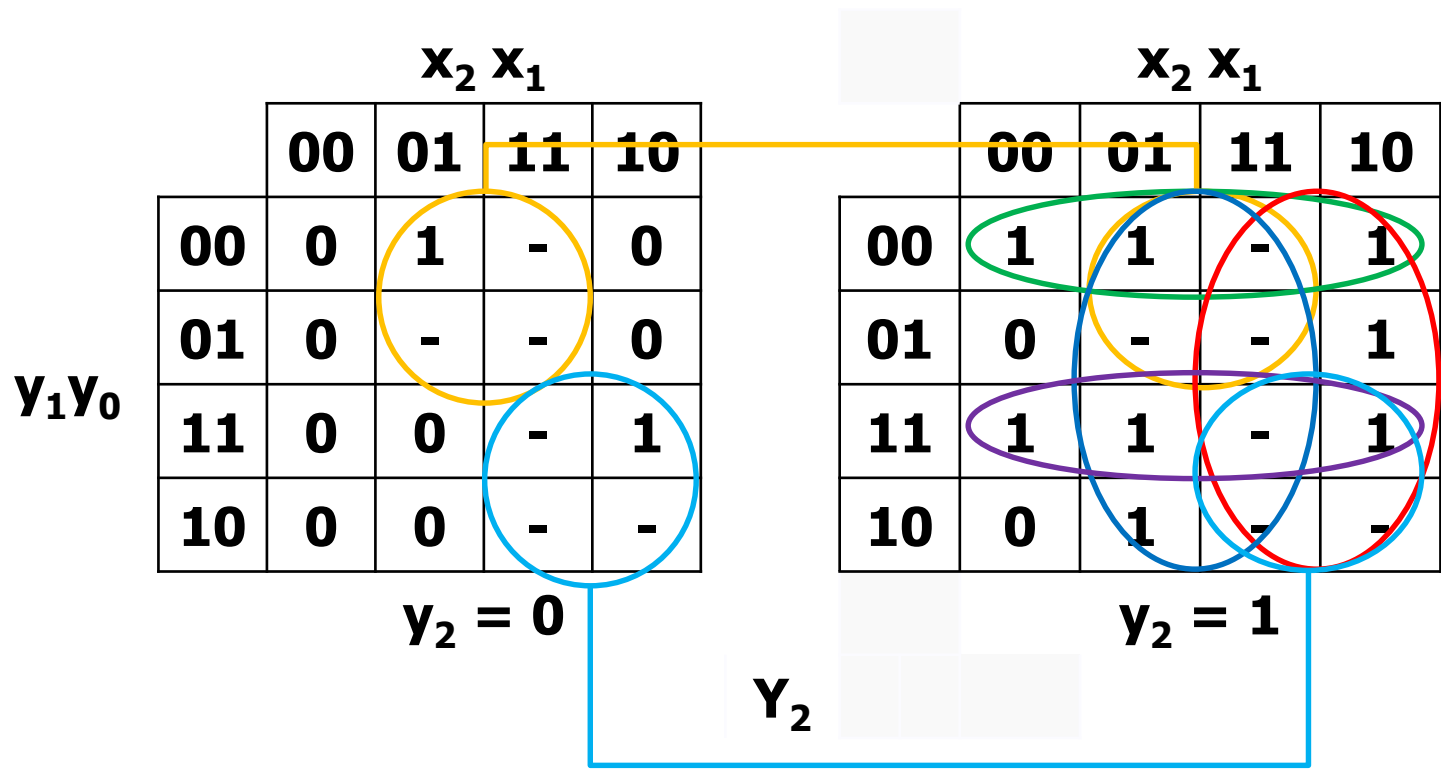

$$Y_2 \text{ (SP)} = y_2 x_2 + y_1' x_1 + y_1 x_2 + y_2 x_1 + y_2 y_1 y_0 + y_2 y_1' y_0'$$

$$Y_2 \text{ (NAND)} = (y_2 \uparrow x_2) \uparrow (y_1' \uparrow x_1) \uparrow (y_1 \uparrow x_2) \uparrow (y_2 \uparrow x_1) \uparrow (y_2 \uparrow y_1 \uparrow y_0) \uparrow (y_2 \uparrow y_1' \uparrow y_0')$$

# Esercizio 2.1

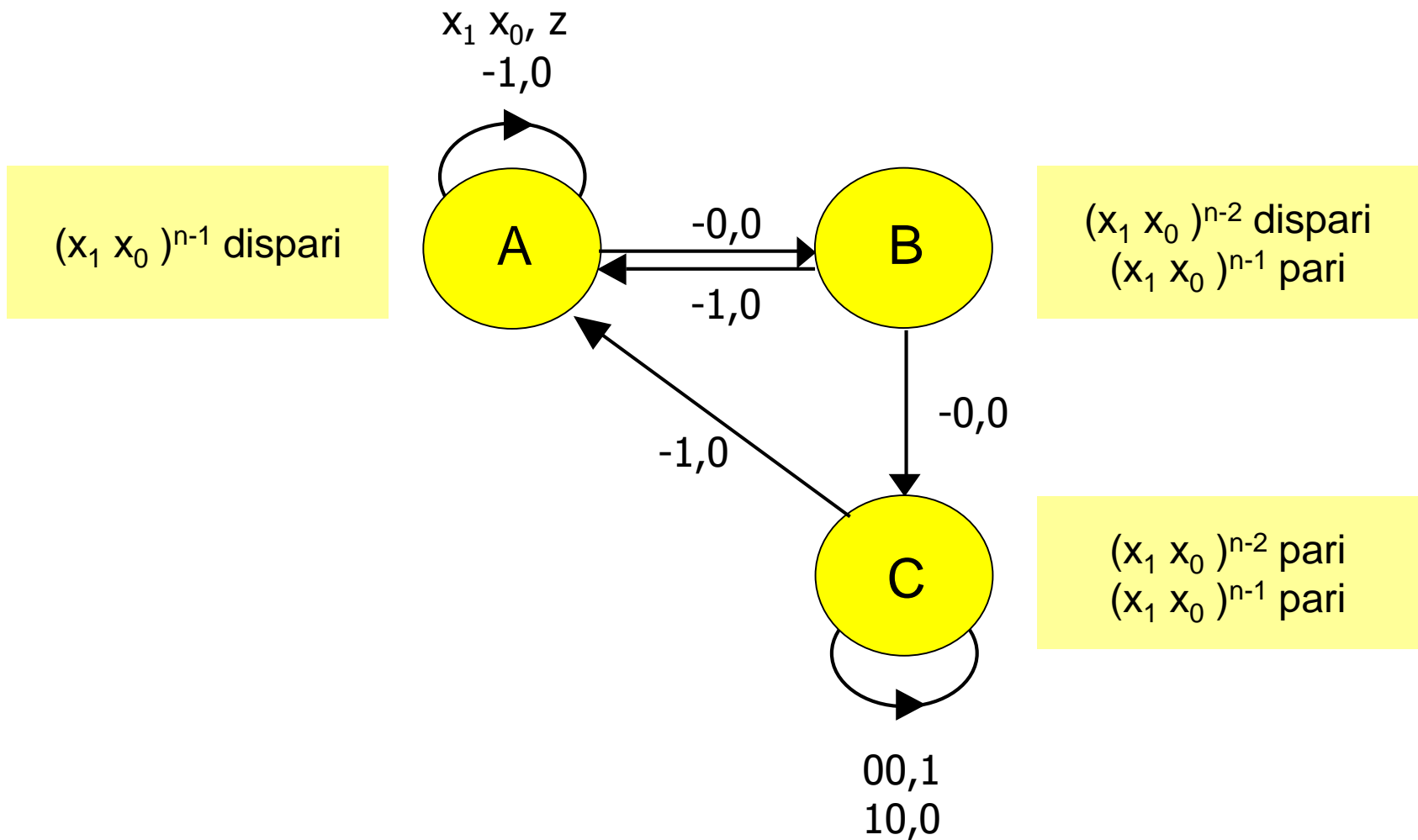

# Esercizio 2.2 – TdF e TdT

$x_1 \ x_0$

		00	01	11	10
<b>s.p.</b>	<b>A</b>	<b>B,0</b>	<b>A,0</b>	<b>A,0</b>	<b>B,0</b>
	<b>B</b>	<b>C,0</b>	<b>A,0</b>	<b>A,0</b>	<b>C,0</b>
	<b>C</b>	<b>C,1</b>	<b>A,0</b>	<b>A,0</b>	<b>C,0</b>

**s.f., z**

$x_1 \ x_0$

		00	01	11	10
$(Q_1 \ Q_0)^n$	<b>A=00</b>	<b>01,0</b>	<b>00,0</b>	<b>00,0</b>	<b>01,0</b>
	<b>B=01</b>	<b>11,0</b>	<b>00,0</b>	<b>00,0</b>	<b>11,0</b>
	<b>C=11</b>	<b>11,1</b>	<b>00,0</b>	<b>00,0</b>	<b>11,0</b>
	<b>10</b>	<b>--,-</b>	<b>--,-</b>	<b>--,-</b>	<b>--,-</b>

$(Q_1 \ Q_0)^{n+1}, z^n$



# Esercizio 2.3 – Sintesi combinatoria

		$x_1 x_0$			
		00	01	11	10
$Q_1 Q_0$	00	0	0	0	0
	01	0	0	0	0
	11	1	0	0	0
	10	-	-	-	-

$$z \text{ (SP)} = x_0' x_1' Q_1$$

$$z \text{ (PS)} = x_0' x_1' Q_1$$

		$x_1 x_0$			
		00	01	11	10
$Q_1 Q_0$	00	0	0	0	0
	01	0	0	0	0
	11	1	0	0	0
	10	-	-	-	-

# Esercizio 2.4 – Flip flop JK

		$x_1 x_0$			
		00	01	11	10
$Q_1 Q_0$	00	0	0	0	0
	01	1	0	0	1
	11	1	0	0	1
	10	-	-	-	-

$Q_1$

		$x_1 x_0$			
		00	01	11	10
$Q_1 Q_0$	00	0	0	0	0
	01	1	0	0	1
	11	-	-	-	-
	10	-	-	-	-

$J_1$

$$J_1 \text{ (PS)} = Q_0 x_0'$$

$$K_1 \text{ (PS)} = x_0$$

		$x_1 x_0$			
		00	01	11	10
$Q_1 Q_0$	00	-	-	-	-
	01	-	-	-	-
	11	0	1	1	0
	10	-	-	-	-

$K_1$

# Esercizio 2.4 – Flip flop JK

		$x_1 x_0$			
		00	01	11	10
$Q_1 Q_0$	00	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
	01	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
	11	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
	10	-	-	-	-

$Q_0$

		$x_1 x_0$			
		00	01	11	10
$Q_1 Q_0$	00	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
	01	-	-	-	-
	11	-	-	-	-
	10	-	-	-	-

$J_0$


$$J_0 \text{ (PS)} = x_0'$$

$$K_0 \text{ (PS)} = x_0$$

		$x_1 x_0$			
		00	01	11	10
$Q_1 Q_0$	00	-	-	-	-
	01	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>
	11	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>
	10	-	-	-	-

$K_0$
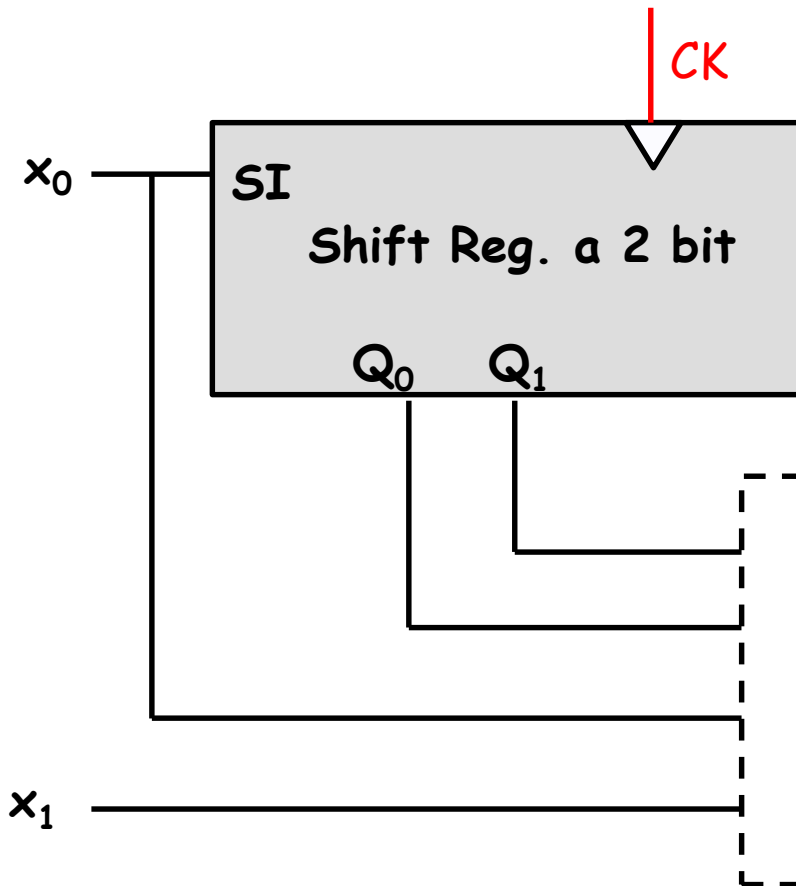
# Esercizio 2.5 – Sintesi con Shift Register



Uscita è 1 quando  
 $x_0^{n-2} = 0$  e  $x_0^{n-1} = 0$   
(ovvero i due numeri precedenti sono pari) e  
 $x_0^n = 0$  e  $x_1^n = 0$   
(ovvero il numero attuale è 0).

$x_0^{n-2}$  e  $x_0^{n-1}$  sono memorizzati rispettivamente in  
 $Q_1^n$  e  $Q_0^n$

La funzione richiesta è quindi il NOR dei 4 segnali.