


# Esercizio 1.1

0 volte 01  
00-10-00  
11-10-00

0 volte 01  
10-00-10  
10-11-10

0 volte 01  
00-10-11  
11-10-11

1 volta 01  
10-00-01  
10-11-01

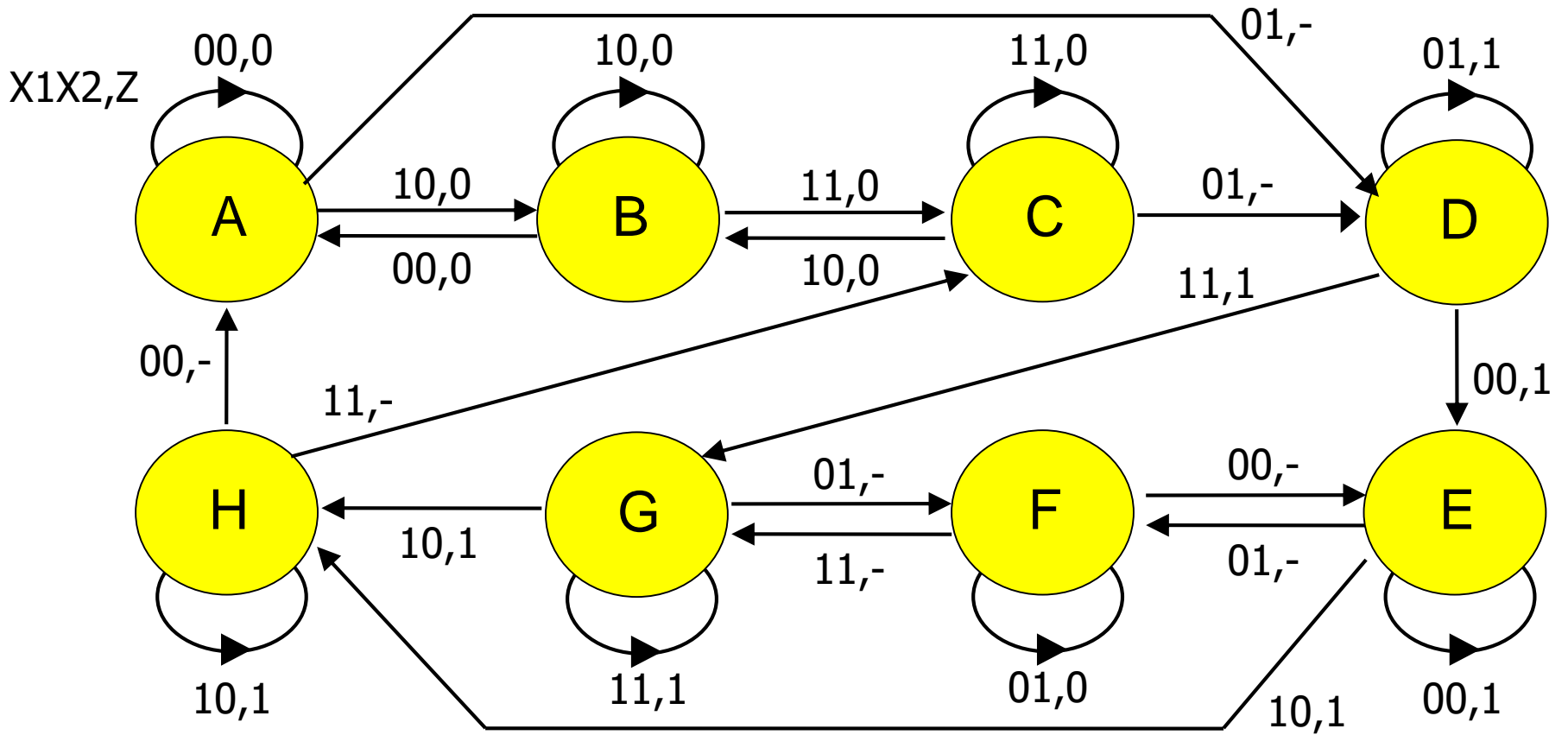

1 volta 01  
01-00-10  
01-11-10

1 volta 01  
00-01-11  
11-01-11

2 volte 01  
01-00-01  
01-11-01

1 volta 01  
00-01-00  
11-01-00

# Esercizio 1.2 – Tabella triangolare e CMC


s.p.

	X1 X2			
	00	01	11	10
A	A,0	D,-	-, -	B,0
B	A,0	-, -	C,0	B,0
C	-, -	D,-	C,0	B,0
D	E,1	D,1	G,1	-, -
E	E,1	F,-	-, -	H,1
F	E,-	F,0	G,-	-, -
G	-, -	F,-	G,1	H,1
H	A,-	-, -	C,-	H,1

s.f., Z

B							
C							
D	/	/	/				
E	/	/	/	DF			
F	AE DF	AE CG	DF CG	/			
G	/	/	/	DF			
H	/	/	/	AE CG	AE	AE CG	CG
	A	B	C	D	E	F	G

AB, AC, BC, D, EF, EG, FG, H

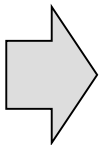

a={ABC}, b={D},  
c={EFG}, h={H}

# Esercizio 1.2 – Tabella triangolare e CMC

		AB			
		00	01	11	10
s.p.	a=ABC	a,0	b,-	a,0	a,0
	b = D	c,1	b,1	c,1	-, -
	c = EFG	c,1	c,0	c,1	d,1
	d = H	a,-	-, -	a,-	d,1

s.f., Z

# Esercizio 1.3 – Grafo adiacenze e TdT

Z	0		1
0	<b>a</b>	→	<b>b</b>
	↑		↓
1	<b>d</b>	←	<b>c</b>

		AB			
		00	01	11	10
s.p.	a = 00	00,0	01,-	00,0	00,0
	b = 01	11,1	01,1	11,1	-, -
	c = 11	11,1	11,0	11,1	10,1
	d = 10	00,-	-, -	00,-	10,1
		s.f., Z			

# Esercizio 1.4 – Mappe di Karnaugh

		X1 X2			
		00	01	11	10
Y <sub>1</sub> Y <sub>0</sub>	00	0	1	0	0
	01	1	1	1	-
	11	1	1	1	0
	10	0	-	0	0

**Y<sub>0</sub>**


$$Y_0 = X_1'X_2 + y_0X_1' + y_1'y_0 + x_2y_0$$

		X1 X2			
		00	01	11	10
Y <sub>1</sub> Y <sub>0</sub>	00	0	-	0	0
	01	1	1	1	-
	11	1	0	1	1
	10	-	-	-	1


**Z**

$$Z = y_1'y_0 + X_2'y_0 + X_1y_0 + y_1X_2'$$

# Esercizio 1.5 – Sintesi con MUX

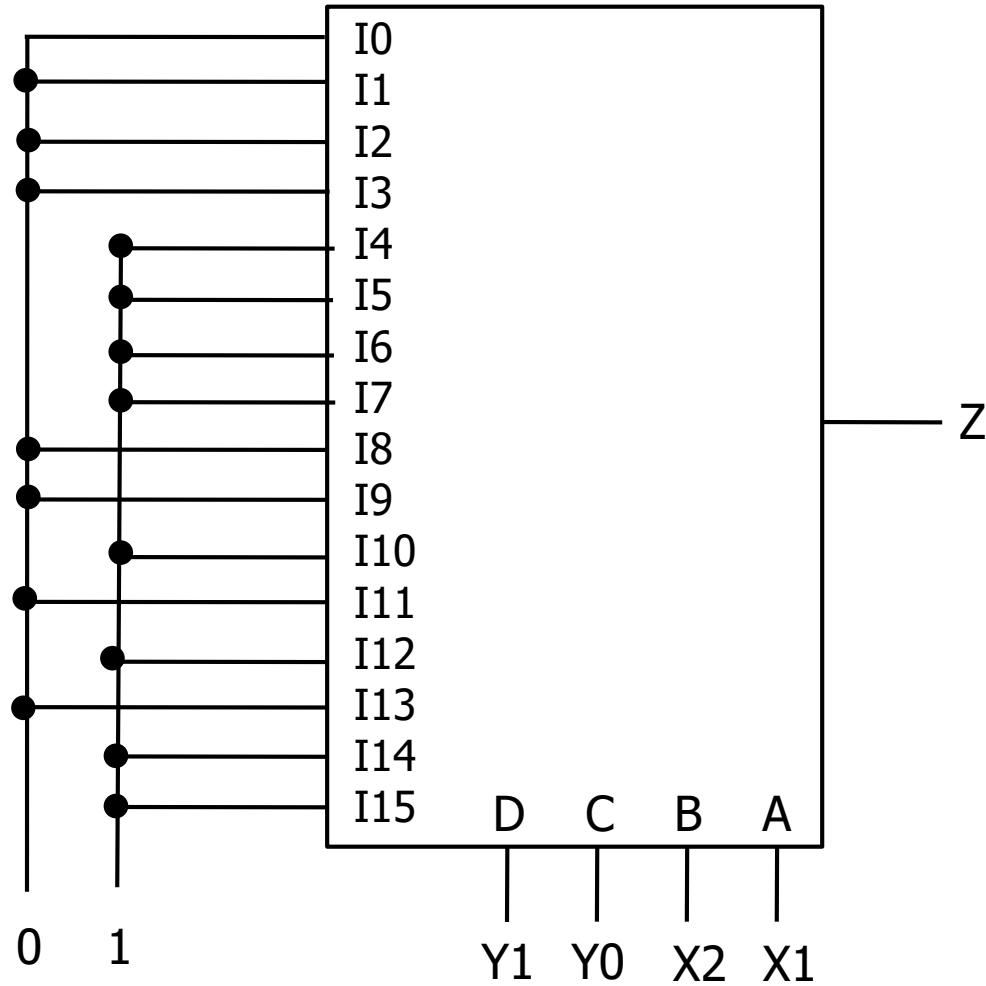

# Esercizio 2.1 – Espressioni

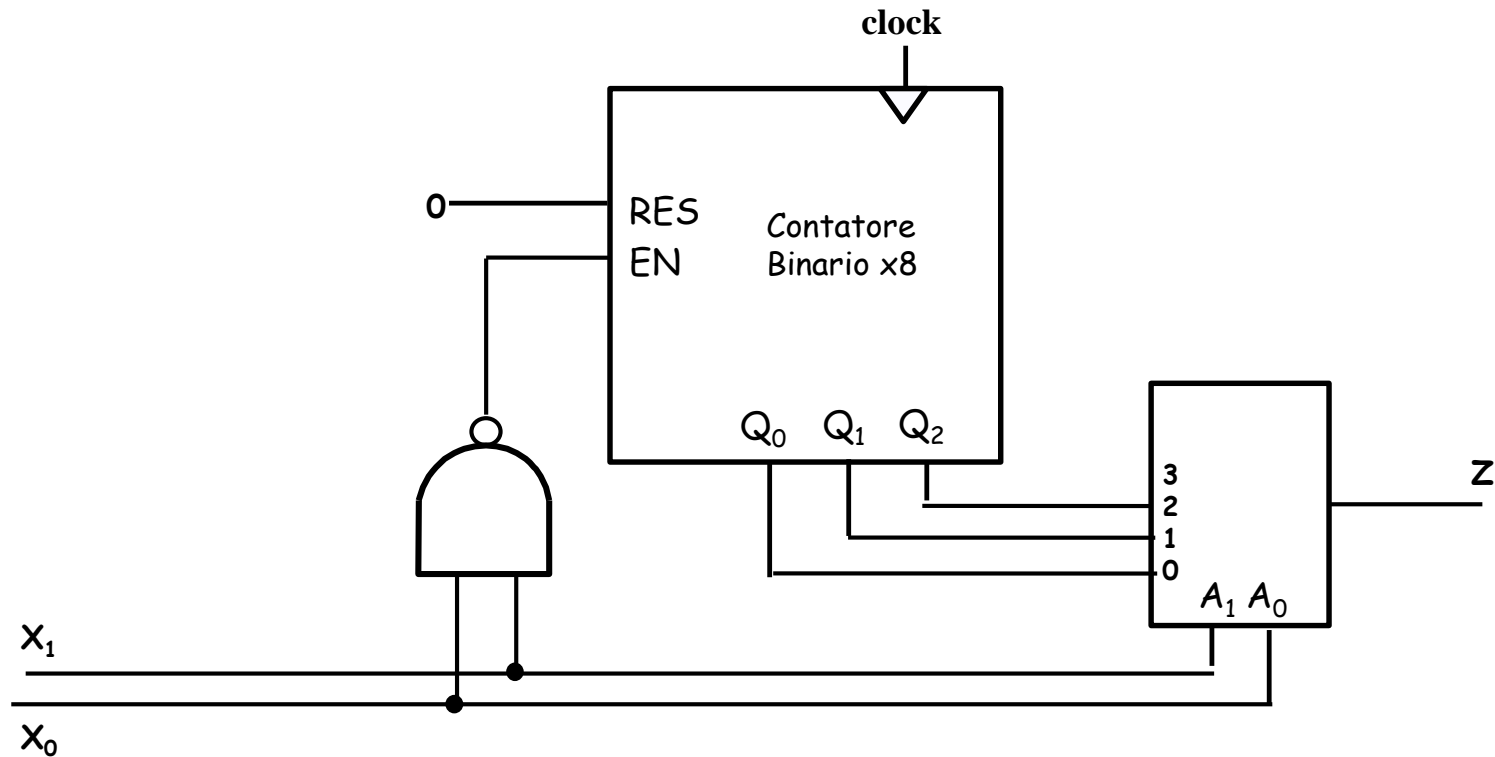

$$Z = X_0' X_1' Q_0 + X_0 X_1' Q_1 + X_0' X_1 Q_2$$

$$RES = 0$$

$$EN = (X_1 X_0)' = X_1' + X_0'$$

# Esercizio 2.2 – Mappa per Z

$$Z = X_0' X_1' Q_0 + X_0 X_1' Q_1 + X_0' X_1 Q_2$$

		$X_1 X_0$			
		00	01	11	10
$Q_1 Q_0$	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	0
	10	0	1	0	0

$Q_2 = 0$

		$X_1 X_0$			
		00	01	11	10
$Q_1 Q_0$	00	0	0	0	1
	01	1	0	0	1
	11	1	1	0	1
	10	0	1	0	1

$Q_2 = 1$

Z



# Esercizio 2.2 – Mappa per RES, EN

$$EN = (X_1 X_0)' = X_1' + X_0'$$

		$X_1 X_0$			
		00	01	11	10
$Q_1 Q_0$	00	1	1	0	1
	01	1	1	0	1
	11	1	1	0	1
	10	1	1	0	1

$Q_2 = 0$

EN

		$X_1 X_0$			
		00	01	11	10
$Q_1 Q_0$	00	1	1	0	1
	01	1	1	0	1
	11	1	1	0	1
	10	1	1	0	1

$Q_2 = 1$

La mappa del segnale RES ha tutti i valori a 0

# Esercizio 2.2 – Tabella con EN,RES,Z

		$X_1 X_0$			
		00	01	11	10
$(Q_2 Q_1 Q_0)^n$	000	10,0	10,0	00,0	10,0
	001	10,1	10,0	00,0	10,0
	011	10,1	10,1	00,0	10,0
	010	10,0	10,1	00,0	10,0
	100	10,0	10,0	00,0	10,1
	101	10,1	10,0	00,0	10,1
	111	10,1	10,1	00,0	10,1
	110	10,0	10,1	00,0	10,1

$(EN,RES)^n, Z^n$

# Esercizio 2.3 – TdT e TdF

		$X_1 X_0$			
		00	01	11	10
$(Q_2 Q_1 Q_0)^n$	000	001,0	001,0	000,0	001,0
	001	010,1	010,0	001,0	010,0
	011	100,1	100,1	011,0	100,0
	010	011,0	011,1	010,0	011,0
	100	101,0	101,0	100,0	101,1
	101	110,1	110,0	101,0	110,1
	111	000,1	000,1	111,0	000,1
	110	111,0	111,1	110,0	111,1


$(Q_2 Q_1 Q_0)^{n+1}, Z^n$

s.p.

		$X_1 X_0$			
		00	01	11	10
0=000	1,0	1,0	0,0	1,0	
1=001	2,1	2,0	1,0	2,0	
3=011	4,1	4,1	3,0	4,0	
2=010	3,0	3,1	2,0	3,0	
4=100	5,0	5,0	4,0	5,1	
5=101	6,1	6,0	5,0	6,1	
7=111	0,1	0,1	7,0	0,1	
6=110	7,0	7,1	6,0	7,1	

s.f.,  $Z^n$

# Esercizio 2.4 – Grafo e comportamento

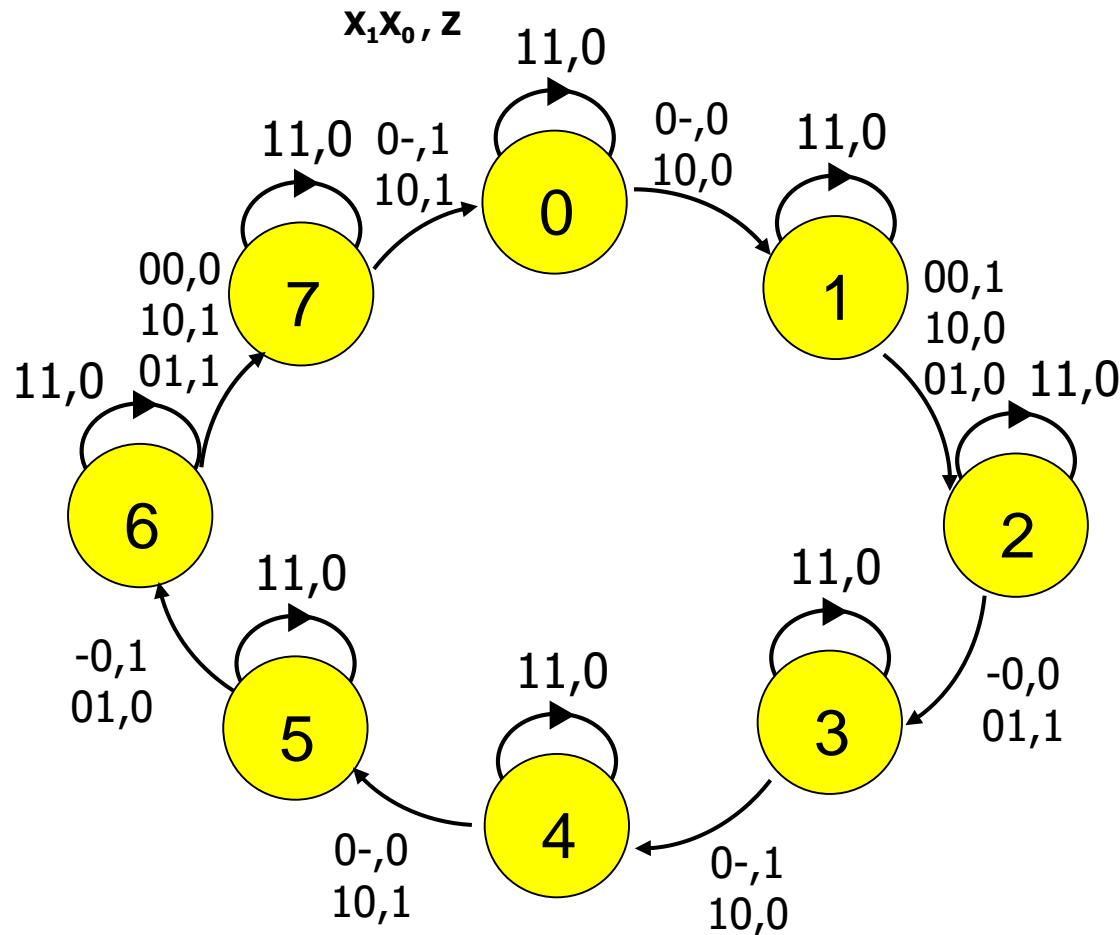

## Comportamento della rete:

Con ingresso pari a  $X_1X_0=00, 01, \text{ e } 10$ , la rete genera sull'uscita  $Z$  un'onda quadra di periodo pari rispettivamente a  $2T, 4T$  e  $8T$  ( $T$ : ciclo di clock)

Con ingresso pari a  $X_1X_0=11$ , la rete genera un segnale costante pari a  $Z=0$ .